
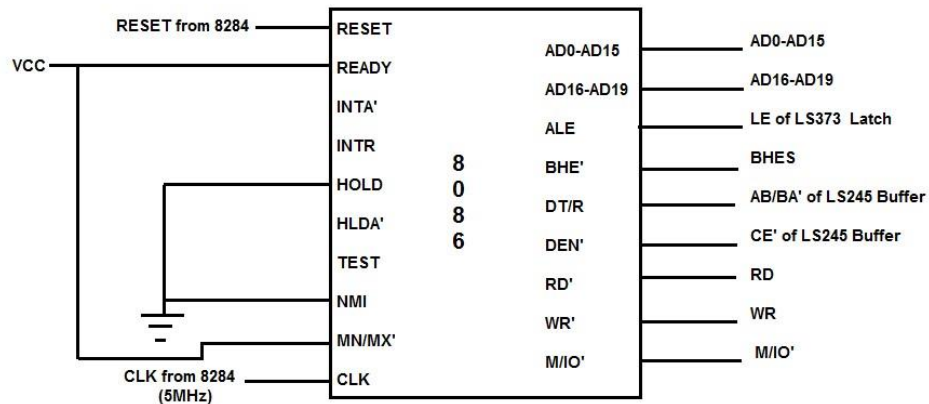


Design Components


1. Connections to 8086 microprocessor


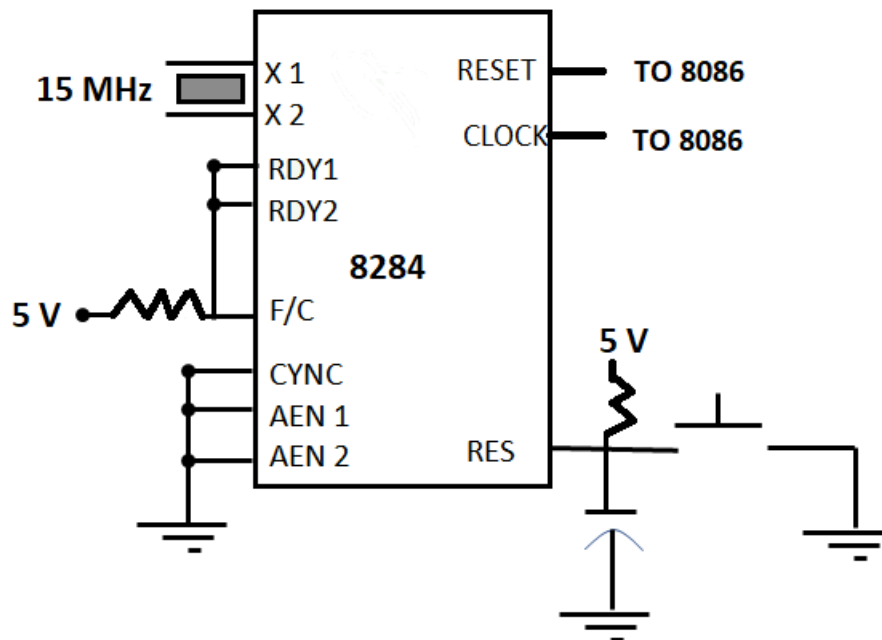


2. Connections to 8284 Clock generator





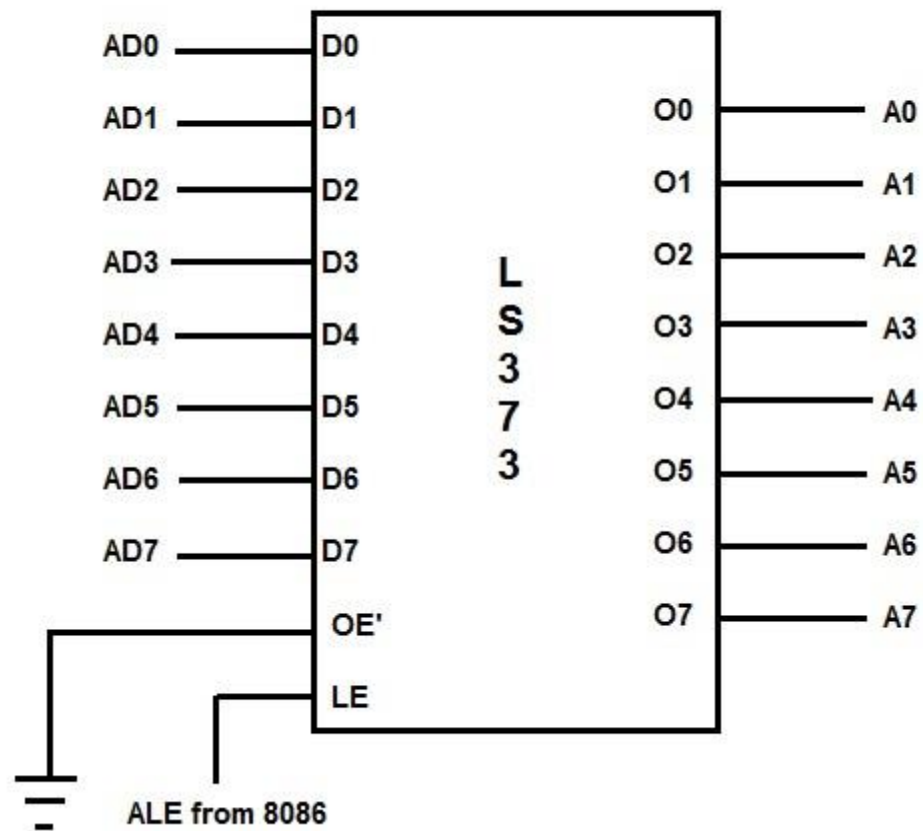3. Address Bus : Connections to 74LS373 Octal Latches




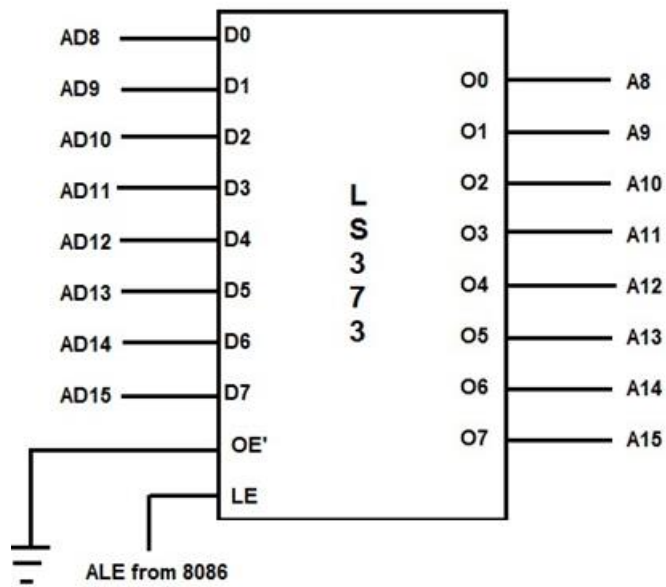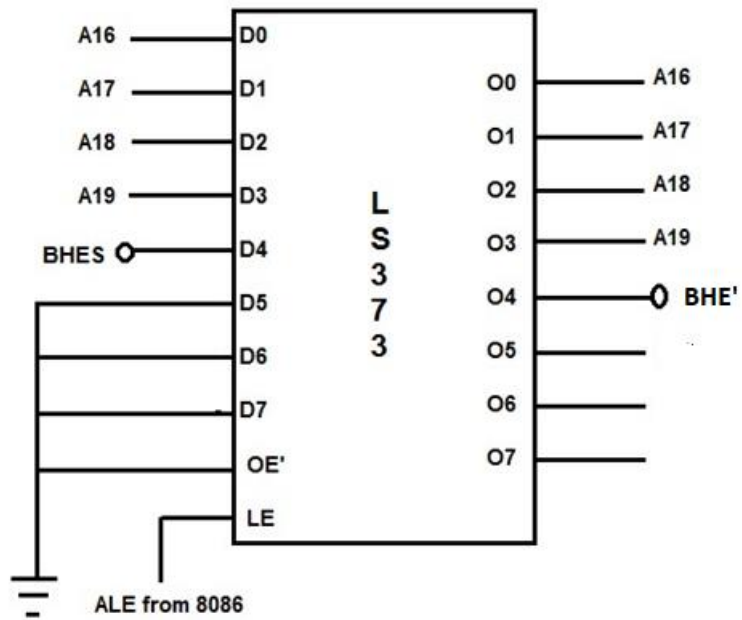

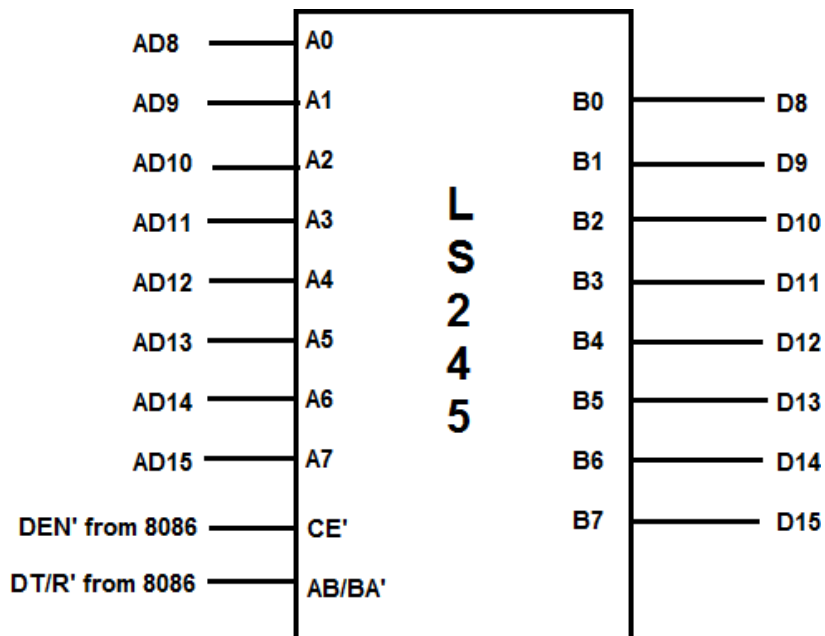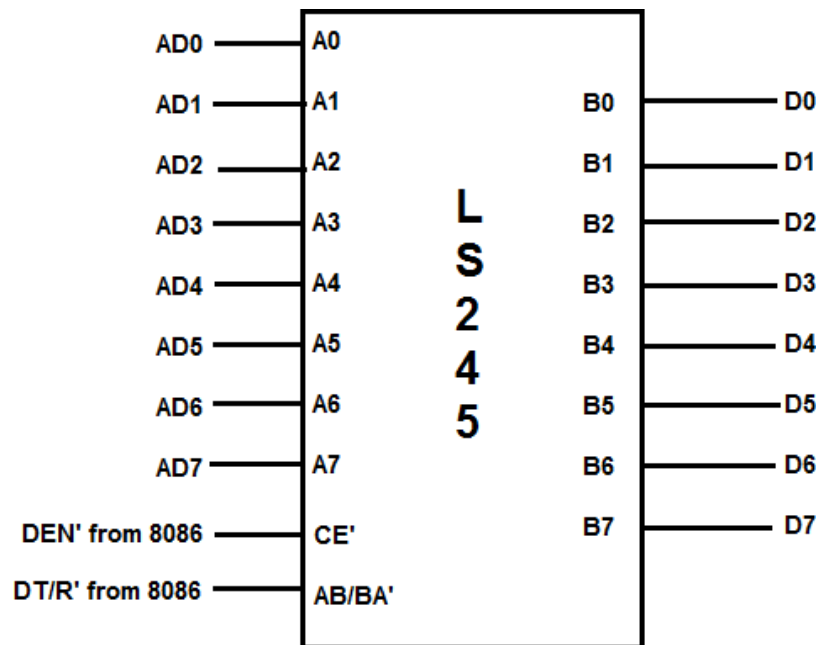
4. Data Bus : Connections to 74LS245 Octal Buffers




5. Memory Decoding Logic

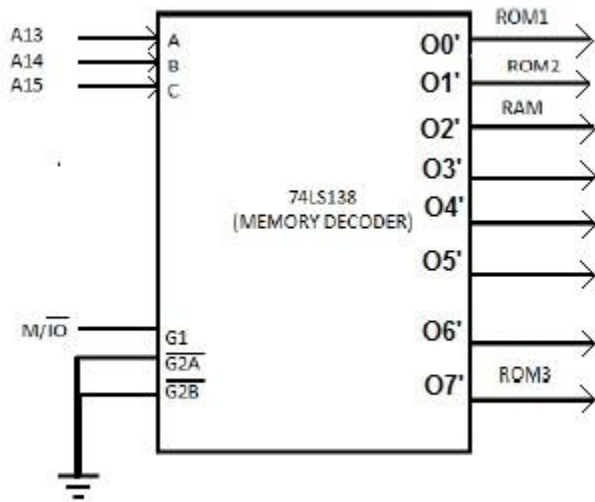


6. I/O Decoding Logic

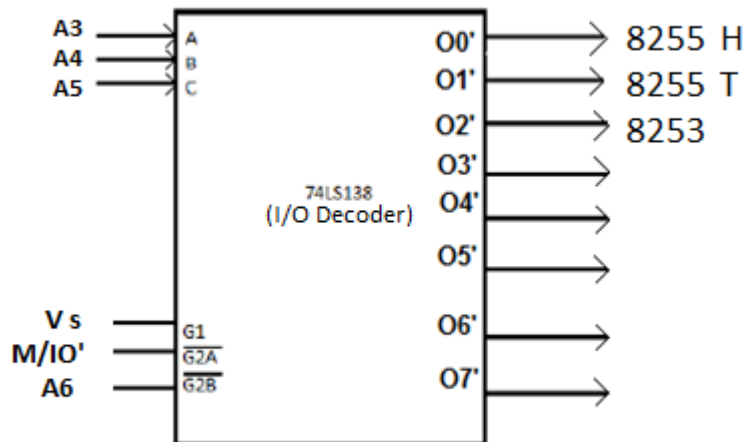


7. Memory Interfacing

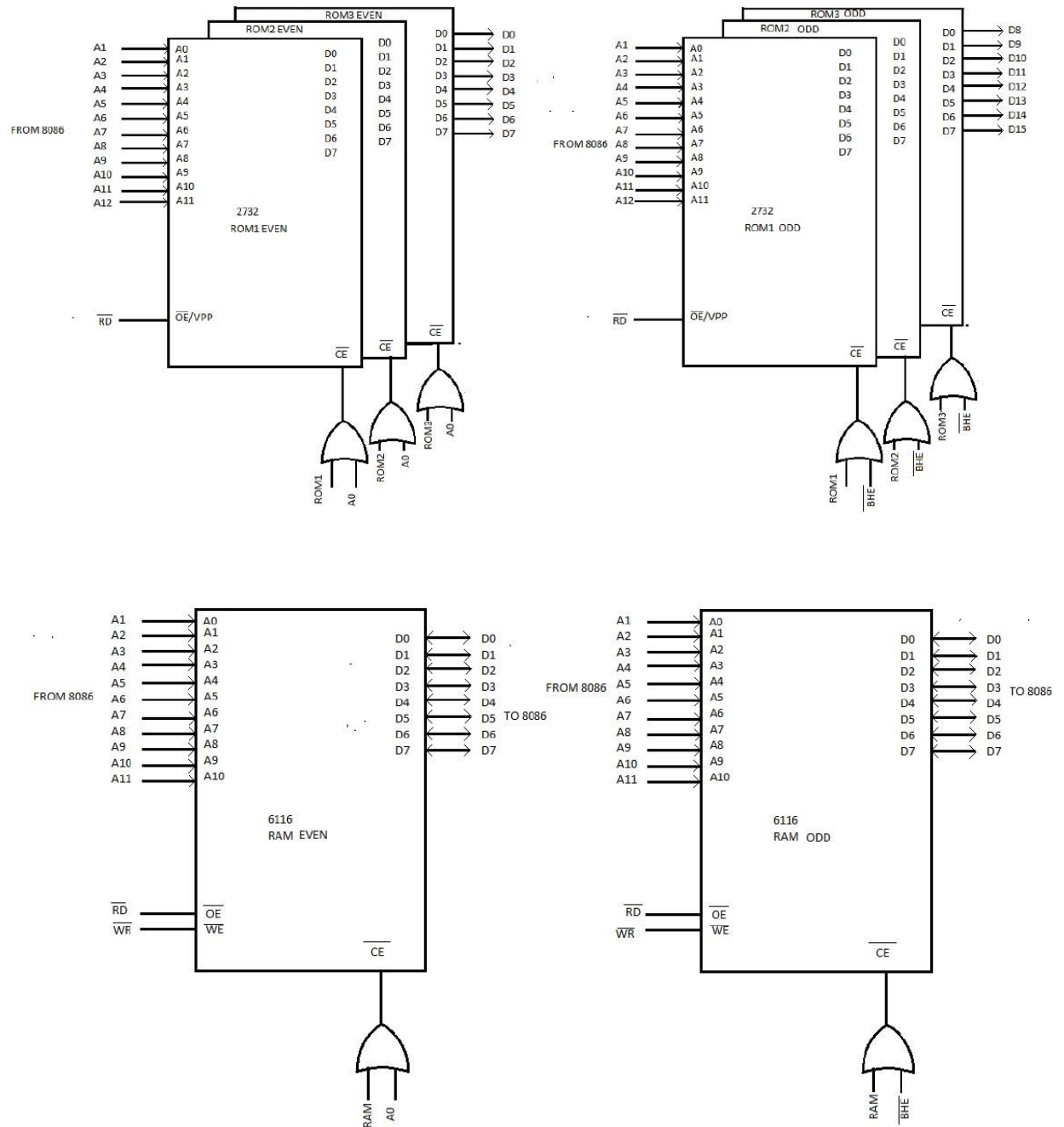


8. Interfacing of ADC(H) with 8255(H)

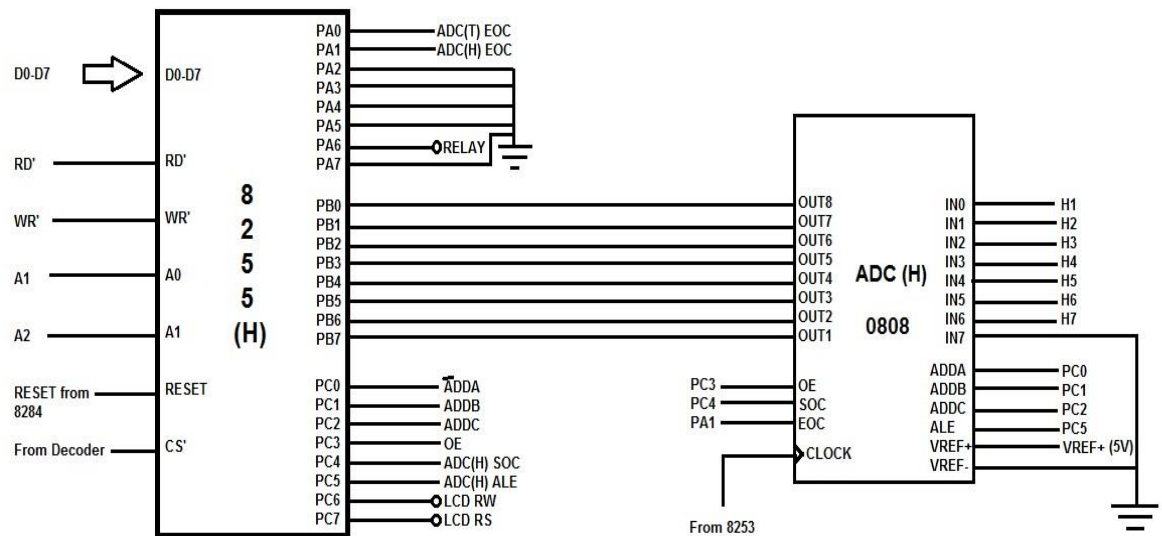



9. Interfacing of ADC(T) with 8255(T)

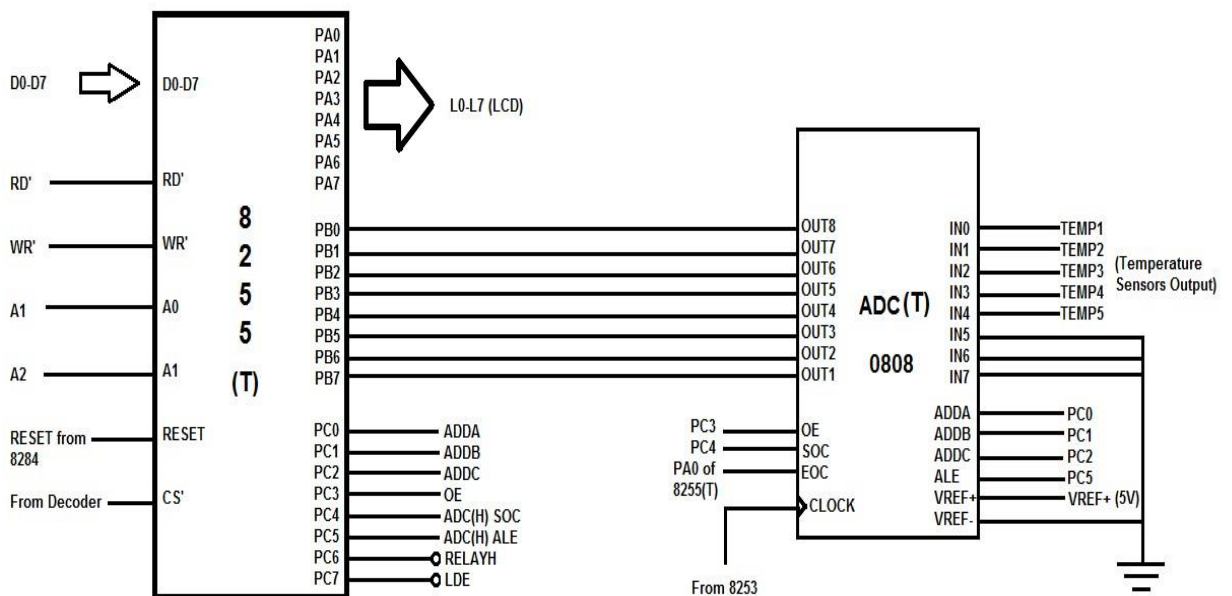

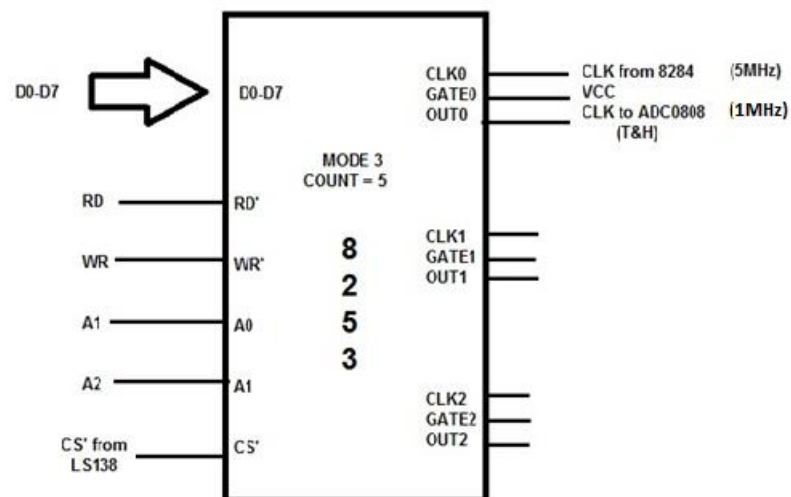
10. Interfacing of 8253 with ADC0808(T) and ADC0808(H)



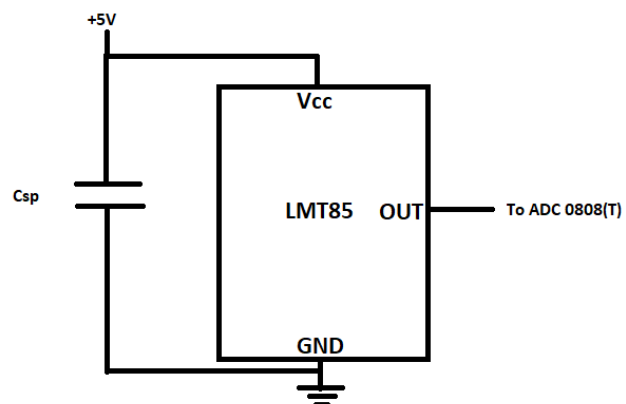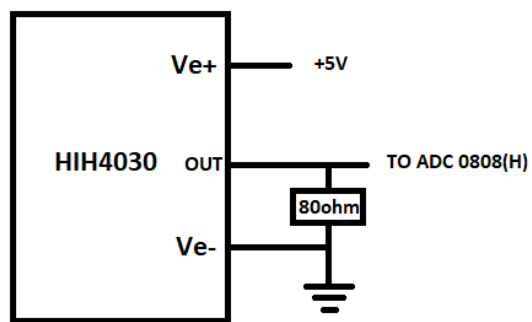11. Connections to Temperature sensor LMT85 and Humidity sensor HIH4030



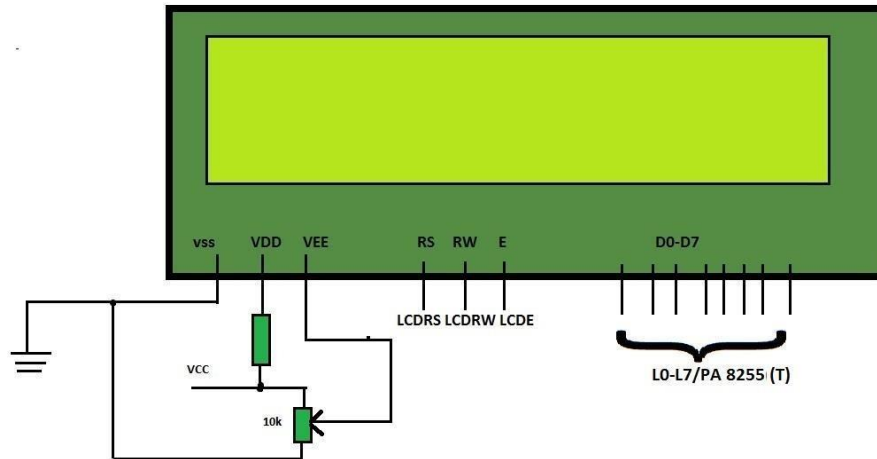12. Interfacing of LCD with 8255(H) and 8255 (T)



13. Simple Relay Interfaced with RELAYH(PC6) from 8255 (T)

